
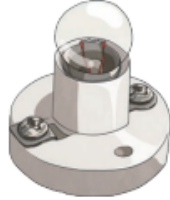
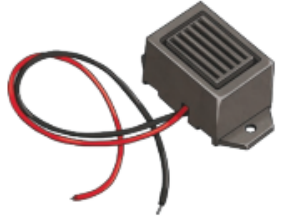

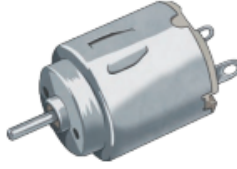




Year 4 - Electricity

| Key Vocabulary | |
|--------------------|--|
| electricity | The flow of an electric current through a material, e.g. from a power source through wires to an appliance . |
| appliances | A piece of equipment or a device designed to perform a particular job, such as a washing machine or mobile phone. |
| battery | A device that stores electrical energy as a chemical. Two or more cells joined together form a battery . |
| circuit | A pathway that electricity can flow around. It is based around wires and a power supply. Examples of components (parts) you can add in to a circuit are bulbs, switches, buzzers and motors. |


| Components (Parts) Vocabulary | | |
|---|--|---|
| cell: Normally, we would call this a battery but scientifically, this is a cell. Two or more cells joined together form a battery .  | bulb: Lights up in a complete circuit .  | buzzer: Makes a noise in a complete circuit .  |
| wires: Used to connect the different components in the circuit together.  | motor: Produces movement in a complete circuit .  | switch: Used to turn other components in the circuit on or off.  |

Series Circuit

A **circuit** where the components are connected in a loop.
Electricity flows through each component in a single pathway.




Complete Circuit

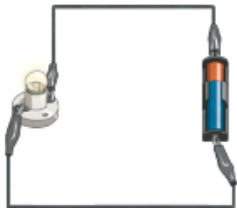


Electricity can flow. The components will work.

Incomplete Circuit


There is a break in the **circuit** that prevents the **electricity** from flowing. The components will not work.



Switches can be used to open or close a **circuit**. When off, a switch 'breaks' the **circuit** to stop the flow of **electricity**. When on, a switch 'completes' the **circuit** and allows the **electricity** to flow.



push button switch



slide switch

Year 4 - Electricity

| Key Vocabulary | |
|----------------------|---|
| mains electricity | Electricity supplied through wires to a building. |
| electrical conductor | A conductor of electricity is a material that will allow electricity to flow through it. |
| electrical insulator | Materials that are electrical insulators do not allow electricity to flow through them. |

| Key Knowledge | |
|---|--|
| Examples of Electrical Conductors | Examples of Electrical Insulators |
| <div style="display: flex; justify-content: space-around; margin-top: 5px;"> water metal </div> | <div style="display: flex; justify-content: space-around; margin-top: 5px;"> wood plastic </div> <div style="display: flex; justify-content: space-around; margin-top: 5px;"> paper rubber glass fabric </div> |

Challenge: What do you think will happen when you add either a conductor or insulator to your circuit?